

If a Silicon diffusion is doped with boron at a concentration of $4.1 \times 10^{16} \text{ cm}^{-3}$, what is the concentration of electrons in this piece of silicon per cm^3 ? Assume $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ at 300°K .

$$(21) n = \frac{n_i^2}{P} = \frac{(1.5 \times 10^{10})^2}{4.1 \times 10^{16}} = 5487.8 \text{ cm}^{-3}$$


If a PN junction is doped with boron at a concentration of $1.4 \times 10^{16} \text{ cm}^{-3}$ and phosphorus at a concentration of $7.5 \times 10^{17} \text{ cm}^{-3}$, then what is the built-in voltage in millivolts for this junction? Assume $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ and $V_t = kT/q = 26 \text{ mV}$ at 300°K .

$$(22) \Phi = 26 \ln\left(\frac{1.4 \times 10^{16} \cdot 7.5 \times 10^{17}}{(1.5 \times 10^{10})^2}\right) = 818.33$$

If a PN junction is doped with boron at a concentration of $5.4 \times 10^{18} \text{ cm}^{-3}$ and phosphorus at a concentration of $1.9 \times 10^{17} \text{ cm}^{-3}$, then what is the built-in voltage in millivolts for this junction? Assume $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ and $V_t = 26 \text{ mV}$ at 300°K .

$$(23) \Phi = 26 \ln\left(\frac{5.4 \times 10^{18} \cdot 1.9 \times 10^{17}}{(1.5 \times 10^{10})^2}\right) = 937.46$$

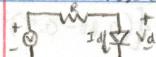If the input voltage to the diode circuit shown, V_i , changes by 1.8V then what will be the change in the diode voltage, V_d , in millivolts? To find the bias point needed for your small signal analysis use the constant voltage model for the diode with $V_d = 0.771\text{mV}$. Use a nominal value for $V_i = 12\text{V}$. Also use $R = 5.7\text{k}\Omega$ and $V_t = 26\text{mV}$.



$$(24) I_d = \frac{V_i - V_d}{R} = \frac{12 - 0.771}{5700} = 0.00197\text{A} = 1.97\text{mA}$$

$$Z = \frac{V_t}{I_d} = \frac{0.026\text{V}}{0.00197\text{A}} = 13.198\Omega$$

$$V_d = \frac{13.198\Omega \cdot V_i}{13.198\Omega + 5700} = \frac{13.198V_i}{5713.198} = 0.00231V_i$$

$$V_d' = 0.771V_i + 0.00231V_i$$

$$V_i = V_i + 1.8\text{V}$$

$$V_d = 0.771 + 0.00231(V_i + 1.8)$$

$$V_d' = 0.771 + 0.00231V_i \pm (0.00231 \cdot 1.8)$$

$$V_d' = V_d \pm 0.004158 \rightarrow 4.158\text{mV} = 4.2\text{mV}$$

For the diode circuit shown, what is the output voltage, V_o , in millivolts? Assume that $I_1 = 10 \times I_2$, and the junction area of D_2 is $7x$ as large as the junction area for D_1 . Use $V_t = 26\text{mV}$.

(25) Vcc

$$I_1 = I_{S1} \left(e^{\frac{V_{o1}}{nVt} - 1} \right)$$

$$V_{o1} \approx I_{S1} e^{\frac{V_{o1}}{nVt}} \quad ① \quad n=1$$


$$I_2 \approx I_{S2} e^{\frac{V_{o2}}{nVt}} \quad ②$$

$$\frac{②}{①} = \frac{I_2}{I_1} = \frac{I_{S2}}{I_{S1}} e^{\frac{V_{o2} - V_{o1}}{Vt}} \rightarrow \frac{1}{10} = 7 e^{\frac{-V_o}{26\text{mV}}} \rightarrow \frac{1}{20} = e^{\frac{-V_o}{26\text{mV}}} \rightarrow$$

$$-4.248 = \frac{-V_o}{0.026} = -0.11046 = -V_o \rightarrow 0.11046 = V_o \rightarrow 110.46\text{mV}$$

For the diode circuit shown, what will the output voltage, V_o , be in volts if the input voltage, V_i , is equal to 5V ? Assume that when a diode is turned on the voltage across it will be 0.7V , and for the batteries use $V_1 = 5.2\text{V}$ and $V_2 = 7.3\text{V}$. Also use $R = 5\text{k}\Omega$.

(26)

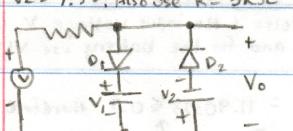

As the input is -5V

A half-wave diode rectifier circuit driven by a 60Hz sine wave with a peak value of 14V. If the load resistance this circuit drives is 4.8k Ω and the ripple voltage at the output is 0.37V_{pp}, then what is the average current in the diode in millamps?

(27)

$$F = 60\text{Hz} \quad R_L = 4800\Omega \quad I_L = \frac{V_p}{R_L} = \frac{14}{4800} = 0.0029\text{A}$$

$$V_p = 14\text{V} \quad V_{pp} = 0.37 \quad I_{D,Avg} = 0.0029\text{A} \left(1 + \pi \left(\sqrt{\frac{2(V_p)}{0.37}}\right)\right) = 0.08215 = 82.15\text{mA}$$

If a MOSFET with $W=5.6\mu\text{m}$ and $L=1.5\mu\text{m}$ is biased in triode, what is the gate-to-drain capacitance, C_{gd} , in femtofarads? Assume the gate dielectric is silicon dioxide with $t_{ox} = 53.6$ angstroms.

(28)

$$C_{gd} = \frac{1}{2} \cdot C_{ox} \cdot W \cdot L \rightarrow \frac{1}{2} \cdot \frac{(3.9 \cdot 8.85 \cdot 10^{-14})}{(53.6 \cdot 10^{-10})} \cdot (5.6 \times 10^{-6}) \cdot (1.5 \times 10^{-6}) = 2.7045 \times 10^{-14} \rightarrow 27.045 \times 10^{-15} \rightarrow 27.045 \text{ femtofarads}$$

If an NMOS FET with $W=7.4\mu\text{m}$ and $L=2.7\mu\text{m}$ is biased in triode with $V_{gs} = 1.2$ and $V_{ds} = 0\text{V}$, what is the on resistance of this MOS switch in ohms? Use: $V_{TN} = 0.5\text{V}$ and $K'n = 100\text{mA/V}^2$

(29)

$$R_{on} = \frac{2V_{ds}}{2I_o} = \frac{1}{K'n \cdot (W/L) \cdot (V_{gs} - V_{TN})} = \frac{1}{(100 \times 10^{-6})(1.4/2.7)(1.2 - 0.5)} = 5212.355\Omega$$

If a PMOS FET with $W/L = 22.7$ has $|V_{gst}| = 0.88$ and $|V_{ds}| = 1.32$, what is the magnitude of the drain current in microamps? Use: $V_{TP} = -0.5\text{V}$, $K'p = 40\text{mA/V}^2$, $X = 0$

$$I_d = \frac{1}{2} \cdot \frac{W}{L} \cdot K'p \cdot [(V_{gs})^2 - |V_{tp}|^2] (1 + (\lambda \cdot |V_{ds}|)) \rightarrow I_d = \frac{1}{2} \cdot 22.7 \cdot (40 \times 10^{-6}) \cdot [(0.88 - 0.5)^2 (1 + (0 \cdot 1.32))] = I_d = 0.000065558 \rightarrow 65.558\text{mA}$$

A full-wave diode rectifier circuit is driven by a 60Hz sine wave with a peak value of 10V. If the load resistance this circuit drives is 9.6k Ω and the ripple voltage at the output is 0.5V_{pp}, then what is the peak current in the diode in millamps?

(31)

$$V_p = 10\text{V} \quad R = 9.6\text{k}\Omega$$

$$V_{pp} = 0.5\text{pp} \quad I_D = \frac{10}{9600} = 0.001041667\text{A}$$

$$I_{peak} = I_D \left[1 + \pi \sqrt{\frac{2V_p}{V_{pp}}}\right] = 0.001041667 \left[1 + \pi \sqrt{\frac{20}{0.5}}\right] = 0.021738 \rightarrow 21.738\text{mA}$$

If the DC bias voltage, V_d , across a reverse biased PN step junction is equal to -2.8V then what is the capacitance of this junction in femtofarads? Assume that C_{j0} for the junction is equal to 288.5 femtofarads. Also assume that the built-in voltage for this junction is equal to 899mV.

(22)

$$\text{mt for step junction} = 1/2$$

$$\text{mt for linear junction} = 1/3$$

$$C_j = \frac{C_{j0}}{(1 - V_d/V_0)^{\text{mt}}} \rightarrow \frac{288.5 \times 10^{-15}}{(1 - (-2.8V)/(899 \times 10^{-3}))^{0.5}} = 142.23 \text{ femtofarads}$$

* (23) If the DC bias current, I_d , for a forward biased PN junction is equal to 0.1 mA then what is the voltage across this diode, V_d , in millivolts? Assume the saturation current for the diode, I_s , is equal to 2fA. Also assume that the thermal voltage is equal to $V_t = 26\text{mV}$. Since the diode current is very sensitive to small changes in the diode voltage, be sure to give your answer to the nearest millivolt.

$$I = 0.1\text{mA} = 0.0001\text{A} \quad I_o = 2\text{fA} = 2 \times 10^{-15}\text{A}$$

$$V_d = ? \quad I = I_o [e^{\frac{V_d}{V_t} - 1}]$$

$$0.0001 = (2 \times 10^{-15}) \left[e^{\frac{V_d}{(26 \times 10^{-3})} - 1} \right] \rightarrow 5 \times 10^{10} = e^{\frac{V_d}{26 \times 10^{-3}} - 1} \rightarrow \ln(5 \times 10^{10}) = \frac{V_d}{0.026} - 1 \rightarrow 24.635 = \frac{V_d}{0.026} - 1$$

$$25.635 = \frac{V_d}{0.026} \rightarrow V_d = 0.66651 = 666.5\text{mV}$$

In the diode circuit shown the value for R was chosen to set the DC bias current, I_d , equal to 4.7mA by using the constant voltage model for the diode with $V_d = 700\text{mV}$. If the actual voltage across the diode is 786mV, then what will be the percent error be in the actual DC bias current compared to the intended value? Use $V_i = 11.2\text{V}$

(24)

$$V_i = I_d R + V_d \quad R = 2234.04\Omega$$

$$11.2 = 0.0047(R) + 0.7 \quad 11.2 = I_d(2234.04) + 0.794$$

$$I_d = 0.004657 \quad \% \text{ error} = \frac{(\text{actual} - \text{intended})}{\text{intended}} \cdot 100$$

$$\% \text{ error} = \frac{0.004657 - 0.0047}{0.0047} \cdot 100 = -0.9489\%$$

(25) For the diode circuit shown, what will the output voltage, V_o , be in volts if the input voltage, V , is a sine wave with an amplitude equal to 5.4V? Assume that when a diode is turned on the voltage across it will be 0.7V.

(26)

$$2(V - V_d) = V_o \quad 2(5.4 - 0.7) = 9.4 \rightarrow -9.4\text{V because of diode direction}$$

$$\text{For the diode circuit shown, what will be the output voltage, } V_o, \text{ be in volts if the input voltage, } V, \text{ is equal to 15V? Assume that when the diode is turned on the voltage across will be 0.7V, and for the battery use } V_i = 5.2\text{V. Also, use } R = 3.2\text{k}\Omega \text{ and } R_L = 12.3\text{k}\Omega.$$


$$V_o = V \cdot \frac{R_L}{(R + R_L)} = 15 \cdot \frac{12300}{3200 + 12300} = 11.90323 < 0.7 \text{ therefore } V_o = V_i + V_d$$

If true the value would be V_o .

$$V_o = 5.2 + 0.7 = 5.9$$

For the diode circuit shown, what will be the output voltage, V_o , be in volts if the input voltage, V , is equal to -2V? Assume that when the diode is turned on the voltage across it will be 0.7V, and for the battery use $V_1 = 8.4V$. Also use $R = 5.9k\Omega$.

(26)

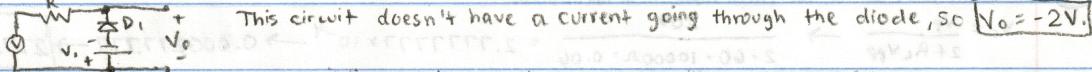

This circuit doesn't have a current going through the diode, so $V_o = -2V$.

A half-wave diode rectifier circuit is driven by a 60Hz sine wave with a peak value of 14V. If the load resistance this circuit drives is $1.6k\Omega$ and 385μF filter capacitor is used, then what is the ripple voltage at the output in millivolts peak-to-peak?

(27)

$$\frac{14V}{0.000385} = (60 \cdot 1600 \cdot V_{pp}) \rightarrow \frac{36363.63636}{(60 \cdot 1600)} = V_{pp} \rightarrow V_{pp} = 0.3787878V \rightarrow 378.78mV$$

A half-wave diode rectifier circuit is driven by a 60Hz sine wave with a peak value of 18V. If the load resistance this circuit drives is $4.2k\Omega$ and the ripple voltage at the output is 0.39 peak-to-peak, then during what percentage of each cycle does the diode conduct?

(28)

The diode in the circuit shown has a reverse breakdown voltage of $V_Z = 6.6V$ at $I_Z = 8.8mA$ and an incremental resistance of $r_Z = 47\Omega$. If this circuit is used as a simple voltage regulator with V_d as the output voltage, then what will the Load Regulation be in mV/mA if a load resistor is attached? Use $V_i = 17V$ and $R = 543\Omega$.

(24)

Current through R: $I = \frac{(V_i - V_d)}{R}$ → $I = \frac{17 - 6.6}{543} = 0.0192A \rightarrow 19.2mA$

$$I_L = I - I_Z \rightarrow I_L = 19.2mA - 8.8mA = 10.4mA$$

The minimum value of $\Delta L = \frac{V_d}{I_L} = \frac{6.6}{10.4mA} = 634.62\Omega$

Change in output $V_o = (R_Z)(-1mA) \rightarrow -47mV$ Load Regulation: $\frac{\Delta V_o}{\Delta I_L} = \frac{-47mV}{1mA} = -47mV/mA$

If a MOSFET with $W = 11.2\mu m$ and $L = 1.2\mu m$ is biased in triode, what is the gate-to-source capacitance, C_{GS} , in femtofarads? $T_{ox} = 36.1$ Angstrom

(28)


$$\frac{1}{2} \cdot C_{ox} \cdot W \cdot L \quad C_{ox} = \frac{3.9 \cdot 8.85 \cdot 10^{-12}}{36.1 \cdot 10^{-10}} = 0.00956$$

$$\frac{1}{2} \cdot 0.00956 \cdot (11.2 \times 10^{-6}) \cdot (1.2 \times 10^{-6}) = 64.25 \text{ femtofarads}$$

For the diode circuit shown, what will the maximum output voltage, V_o , be in volts if the input voltage, V , is a square wave which varies between +3.6V and -8.6V? Assume that when the diode is turned on the voltage across it will be 0.7V.

(25)

$$3.6V - (-8.6) - 0.7 = 11.5V$$

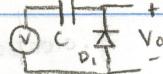

A full-wave diode rectifier circuit is driven by a 60Hz sine wave with a peak value of 10V. If the load resistance this circuit drives is $4.4k\Omega$ and the ripple voltage at the output is 0.13V_{pp}, then what is the average current in the diode in millamps?

(31)

$$I_{DAVG} = \frac{V_p}{R_L} \left(1 + \pi \left(\sqrt{\frac{V_p}{2V_{pp}}} \right) \right) \rightarrow \frac{10}{4400} \left(1 + \pi \left(\sqrt{\frac{10}{2 \cdot 0.13}} \right) \right) = 0.04655A \rightarrow 46.55mA$$

If the DC bias voltage, V_{d1} , across a forward biased PN junction is equal to 732mV then what is the current flowing through this diode, I_d , in millamps? Assume that the saturation current for the diode, I_s , is equal to 1femtoamp. Also assume that the thermal voltage is equal to $V_t = 26mV$.

(23)

$$V_d = 732mV = 0.732V \quad V_t = 26mV = 0.026V \quad I_d = I_s [e^{\frac{V_d}{V_t}} - 1] \quad I_d = (1 \times 10^{-15}) [e^{0.732/0.026} - 1] = 0.0016867 = 1.686mA$$


The diode in the circuit shown has a reverse breakdown voltage $V_Z = 6.8V$ at $I_Z = 1.4mA$ and an incremental resistance of $r_Z = 97\Omega$. If this circuit is used as a simple voltage regulator with V_d as the output voltage, then what will the Line Regulation be in mV/V? Use $V_i = 18.5V$ and $R = 731\Omega$.

(24)

$$\Delta V_o = \frac{r_Z}{(r_Z + R)} = \frac{97}{(97 + 731)} = 0.117149 \rightarrow 117.149 mV/V$$

For the diode circuit shown, what will the maximum output voltage, V_o , be in volts if the input voltage, V , is a square wave which varies between +6.0V and -7.2V? Assume that when the diode is turned on the voltage across it will be 0.7V.

(25)

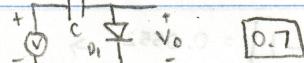


If a NMOS FET with $W/L = 27.6$ has $V_{gs} = 0.95$ and $V_{ds} = 1.53$, what is the drain current in microamps? Use $V_{TN} = 0.5V$, $k'n = 100\mu A/V^2$

(30)

$$I_D = \frac{1}{2} k'n \left(\frac{W}{L} \right) (V_{gs} - V_{tn})^2 (1 + \gamma V_{os}) \rightarrow \frac{1}{2} (100 \times 10^{-6}) (27.6) (0.95 - 0.5)^2 (1 + (0.22 \cdot 1.53)) = 0.0003735A \rightarrow 373.5mA$$

SQUARE
WAVE

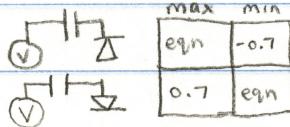

MAX	MIN
eqn	-0.7
0.7	eqn

$$V_{D,0} = V_{D,1} = V_i - V_{D,0}$$

(24)

The diode in the circuit shown has a reverse breakdown voltage $V_Z = 6.0V$ at $I_Z = 7.9mA$ and an incremental resistance of $r_Z = 95\Omega$. What will the voltage across the diode, V_d , be in volts if $V_i = 11.6V$ and $R = 602\Omega$?



$$V_{Z0} = V_Z - I_Z r_Z$$

$$6 - (0.0079)(95) = 5.2495V$$

$$V_d = \left[\frac{V_i - V_{Z0}}{R + r_Z} \right] r_Z + V_{Z0} \rightarrow \left[\frac{11.6 - 5.2495}{602 + 95} \right] 95 + 5.2495$$

$$\boxed{V_d = 6.12V}$$