

**Started on** Thursday, 31 August 2017, 2:01 PM

**State** Finished

**Completed on** Friday, 8 September 2017, 1:32 PM


**Time taken** 7 days 23 hours

**Grade** 5.0 out of 10.0 (50%)

**Question 1**

Correct

Mark 1.0 out of 1.0

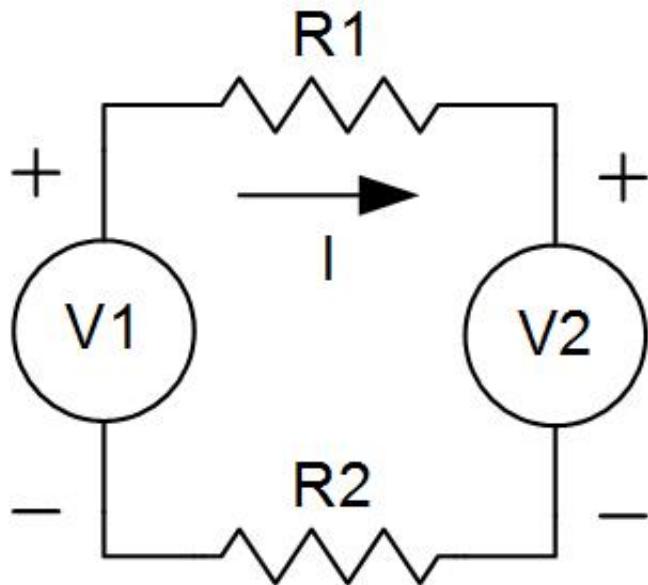

For the circuit shown, what is the value of the current  $I$  in milliamps? Use:  $V_1 = 6.9V$ ,  $V_2 = 8.5V$ ,  $R_1 = 6.7k\Omega$  and  $R_2 = 17.0k\Omega$ .

Answer: -0.0675



The correct answer is: -0.068

**Correct**

Marks for this submission: 1.0/1.0.

**Question 2**

Correct

Mark 0.0 out of 1.0

What is the phase in degrees of the complex impedance, Z, for a  $79\Omega$  resistor in series with a  $5.2\text{pF}$  capacitor at  $92.7\text{MHz}$ ?

Answer: -76.54



The correct answer is: -76.54


**Correct**

Marks for this submission: 1.0/1.0. Accounting for previous tries, this gives **0.0/1.0**.

**Question 3**

Correct

Mark 1.0 out of 1.0

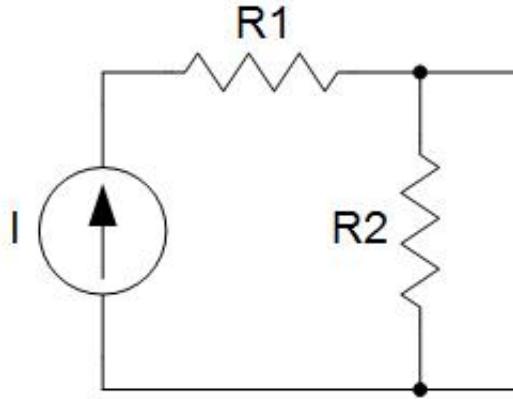

Use Norton's Theorem to find the value of the short circuit output current for the circuit shown in millamps. Use:  $I = 2.1\text{mA}$ ,  $R1 = 38.1\text{k}\Omega$  and  $R2 = 45.8\text{k}\Omega$ .

Answer: 2.1



The correct answer is: 2.10


**Correct**

Marks for this submission: 1.0/1.0.

**Question 4**

Correct

Mark 1.0 out of 1.0

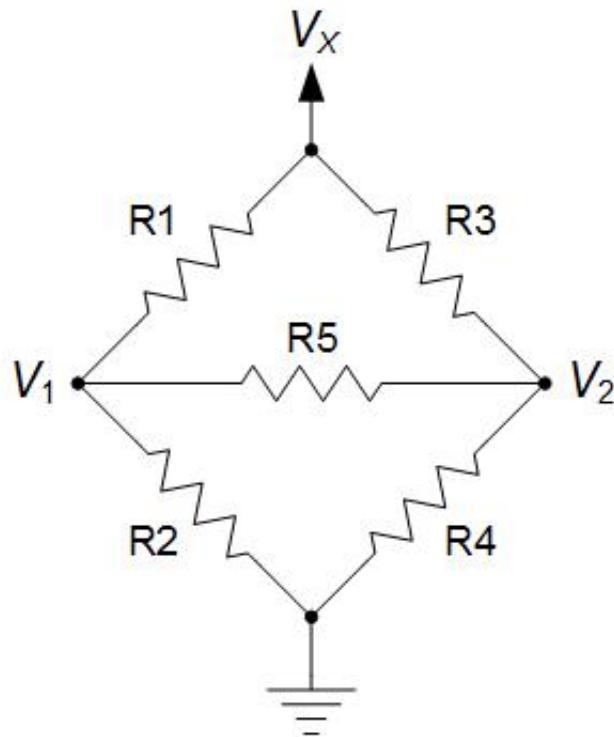

For the bridge circuit shown what is  $V_{12}$ , the voltage across  $R_5$ , in millivolts?  
(Hint: Use Thevenin equivalents to solve this problem more easily.) Use:  $V_x = 3.2V$ ,  $R_1 = 4.5k\Omega$ ,  $R_2 = 8.4k\Omega$ ,  $R_3 = 5.1k\Omega$ ,  $R_4 = 7.3k\Omega$  and  $R_5 = 7.6k\Omega$ .

Answer: 112.34



The correct answer is: 112.2

**Correct**

Marks for this submission: 1.0/1.0.

**Question 5**

Correct

Mark 1.0 out of 1.0

In the phrase “ELI the ICE man” the letter I stands for :

Select one:

- a. Voltage
- b. Energy
- c. None of these
- d. Power
- e. Current ✓

The correct answer is: Current

**Correct**

Marks for this submission: 1.0/1.0.

**Question 6**

Correct

Mark 0.0 out of 1.0

Capacitors in series can be combined to find the total equivalent capacitance by :

Select one:

- a. Adding the capacitances together
- b. Adding the reciprocal of each capacitance together
- c. Multiplying the capacitances together
- d. None of the these
- e. Taking the reciprocal of the sum of the reciprocals of each capacitance ✓

The correct answer is: Taking the reciprocal of the sum of the reciprocals of each capacitance

**Correct**Marks for this submission: 1.0/1.0. Accounting for previous tries, this gives **0.0/1.0**.

**Question 7**

Correct

Mark 0.0 out of 1.0

If a voltage source is applied across two resistors in series, R<sub>1</sub> and R<sub>2</sub>, and less of the voltage appears across R<sub>1</sub> than across R<sub>2</sub>, then :

Select one:

- a. R<sub>1</sub> has a higher resistance than R<sub>2</sub>
- b. R<sub>1</sub> has a lower resistance than R<sub>2</sub> ✓
- c. None of these
- d. R<sub>1</sub> has the same resistance as R<sub>2</sub>
- e. No way to determine

The correct answer is: R<sub>1</sub> has a lower resistance than R<sub>2</sub>

**Correct**

Marks for this submission: 1.0/1.0. Accounting for previous tries, this gives **0.0/1.0**.

**Question 8**

Correct

Mark 1.0 out of 1.0

For an inductor, the phase of the voltage lags the current by 90 degrees.

Select one:

- True
- False ✓

The correct answer is 'False'.

**Correct**

Marks for this submission: 1.0/1.0.

**Question 9**

Correct

Mark 0.0 out of 1.0

The power dissipated by an ideal inductor is equal to the square of the voltage across the inductor divided by the inductance.

Select one:

- True
- False ✓

The correct answer is 'False'.

**Correct**

Marks for this submission: 1.0/1.0. Accounting for previous tries, this gives **0.0/1.0**.

**Question 10**

Correct

Mark 0.0 out of 1.0

The voltage across an ideal voltage source increases as the current through it increases.

Select one:

- True
- False ✓


The correct answer is 'False'.

**Correct**

Marks for this submission: 1.0/1.0. Accounting for previous tries, this gives **0.0/1.0**.

Quiz 1A-1

(4)

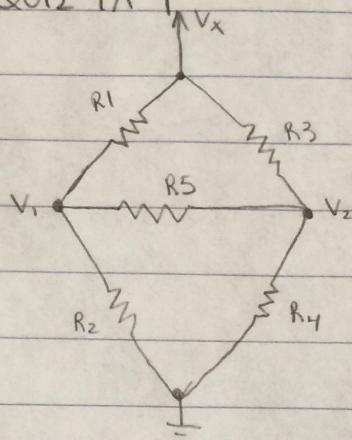

$$R_1 = 4.5 \text{ k}\Omega = 4500 \Omega$$

$$R_2 = 8.4 \text{ k}\Omega = 8400 \Omega$$

$$R_3 = 5.1 \text{ k}\Omega = 5100 \Omega$$

$$R_4 = 7.3 \text{ k}\Omega = 7300 \Omega$$

$$R_5 = 7.6 \text{ k}\Omega = 7600 \Omega$$

$$V_x = 3.2 \text{ V}$$

Voltage across R5 in millivolts?


$$V_{th} = 3.2 \text{ V} \left[ \frac{\frac{5.1 \text{ k}\Omega}{5.1 + 7.3}}{0.41129} - \frac{\frac{4.5 \text{ k}\Omega}{4.5 + 8.4}}{0.3488} \right] = 0.199968 = 0.2 \text{ V}$$

$$R_{th} = \left( \frac{(4.5)(8.4)}{4.5 + 8.4} + \frac{(5.1)(7.3)}{5.1 + 7.3} \right) = 5.93 \text{ k}\Omega$$

$$2.93 + 3.0024$$

$$V_{12} = \frac{V_{th}}{R_{th} + R_5} \times R_5 = \frac{0.2 \text{ V}}{5.93 \text{ k}\Omega + 7.6 \text{ k}\Omega} \times 7.6 \text{ k}\Omega = 0.11234 \text{ V} = 112.34 \text{ mV}$$

(3)

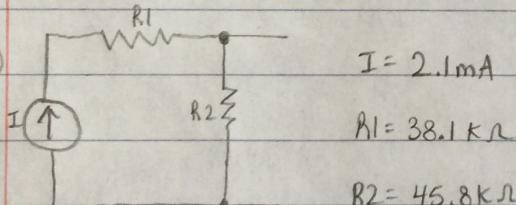


$$I = 2.1 \text{ mA}$$

Norton's Theorem short circuit current

$$R_1 = 38.1 \text{ k}\Omega$$

$$R_2 = 45.8 \text{ k}\Omega$$

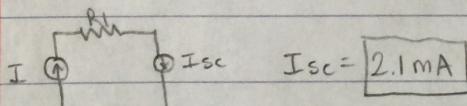


② Phase in degrees of the complex impedance Z

79 Ω      5.2 pF      @ 92.7 MHz

R = 79 Ω      C = 5.2 pF      f = 92.7 MHz

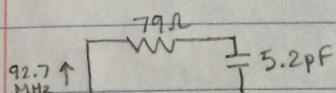
$$\omega = 2\pi f = 582.45 \times 10^6 \text{ rad/sec}$$



$$Z = 79 \Omega - \frac{j}{(582.45 \times 10^6)(5.2 \times 10^{-12})} \rightarrow 79 \Omega - \frac{j}{(582.45 \cdot 5.2 \times 10^{-6})} \rightarrow 79 - j330.17$$

$$Z = 79 - j(330.17) \rightarrow |Z| = \sqrt{(79)^2 + (330.17)^2} = 339.48965 \approx 339.49 \Omega$$
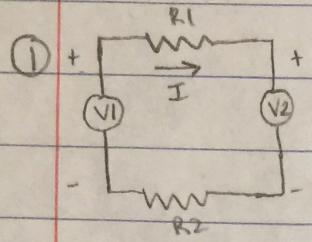
$$\theta = \arctan \left( \frac{-330.17}{79} \right) = -76.54^\circ$$



$$V_1 = 6.9 \text{ V}$$

$$R_1 = 6.7 \text{ k}\Omega = 6700\Omega$$

$$V_2 = 8.5 \text{ V}$$

$$R_2 = 17 \text{ k}\Omega = 17000\Omega$$

$$V = IR$$

$$I = \frac{6.9 - 8.5}{6700 + 17000} = \frac{-1.6 \text{ V}}{23700\Omega} = -0.000067511 \text{ A} = 0.0675 \text{ mA}$$